
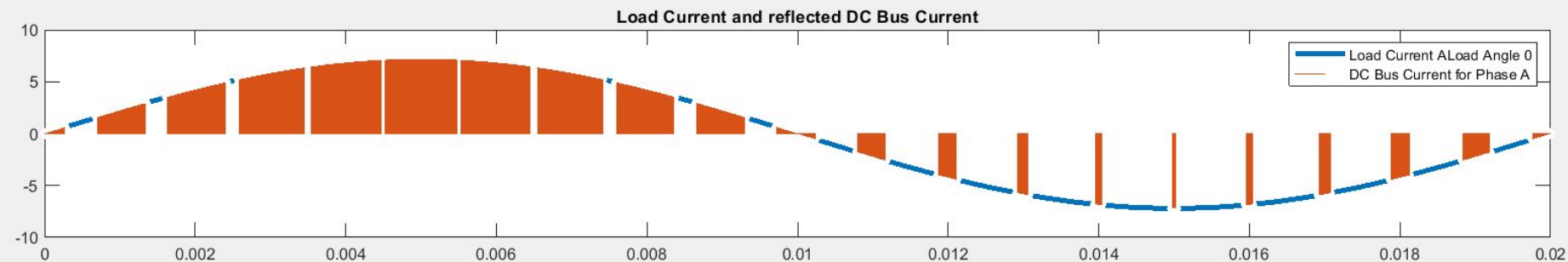
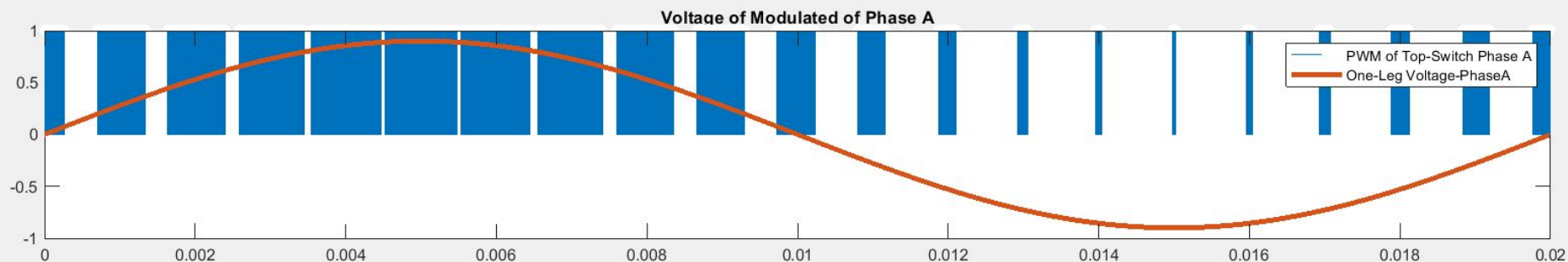


DC BUS MODELLING


- Switching Modelling
- Capacitor Response Modelling
 - Rectifier Modelling




Geometric Model

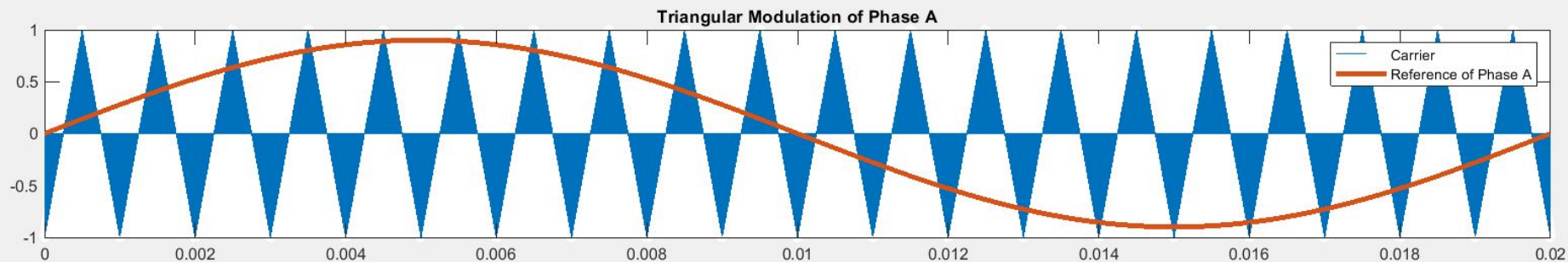- In literature, the model is used for confirming the mathematical model and visualization of the DC bus current as expected.
- Power factor and DC BUS ripples can be linked.







Capacitor current Load Angle with 0

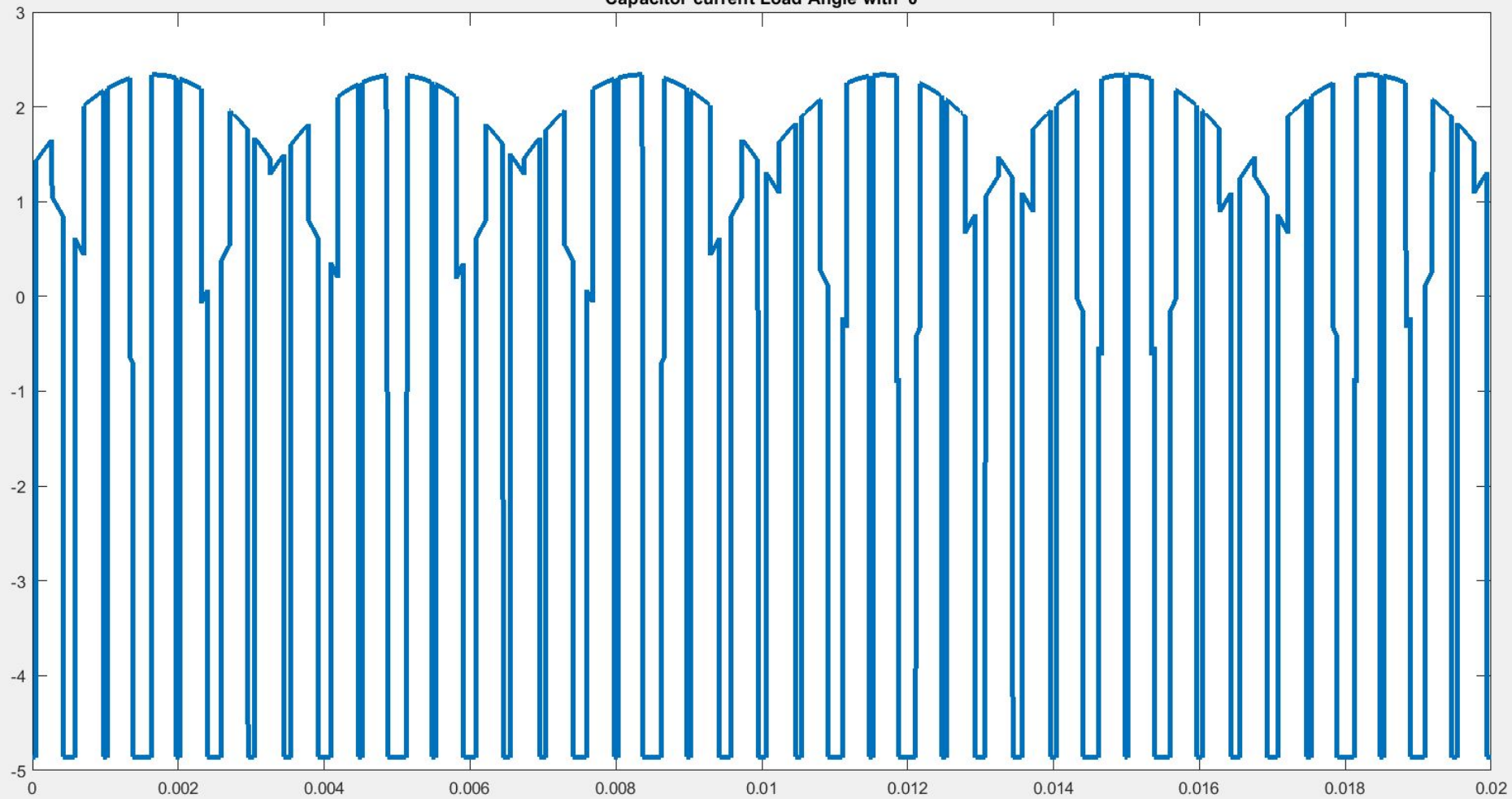


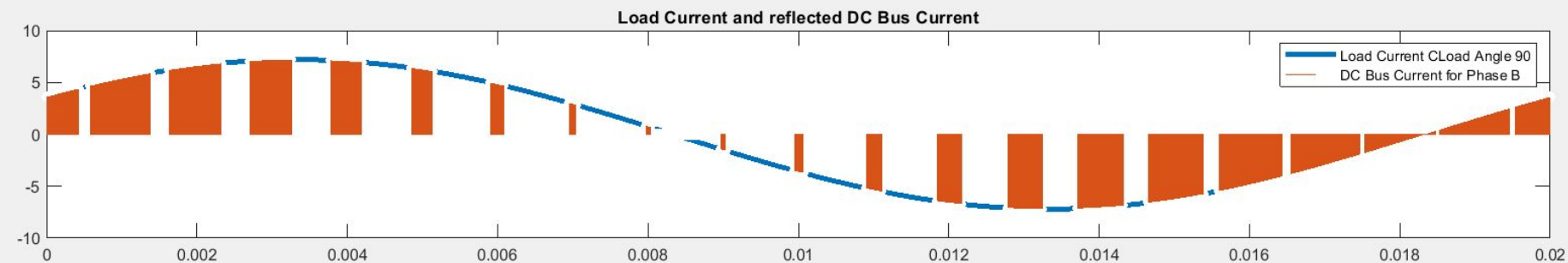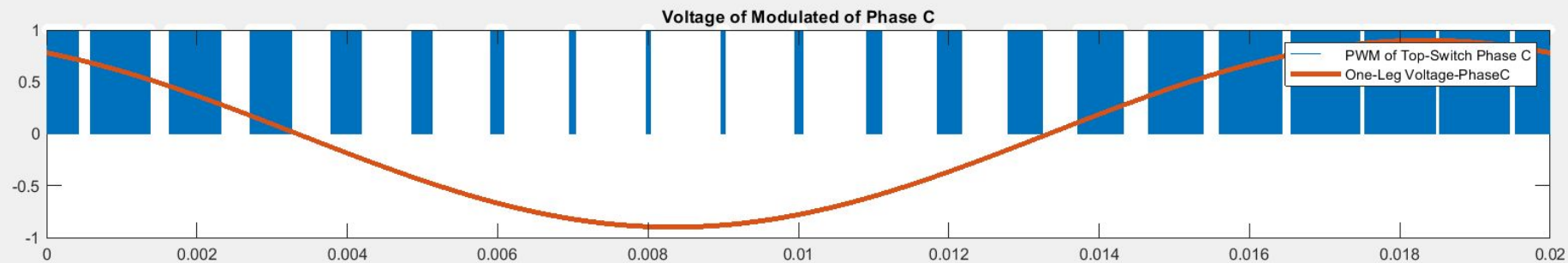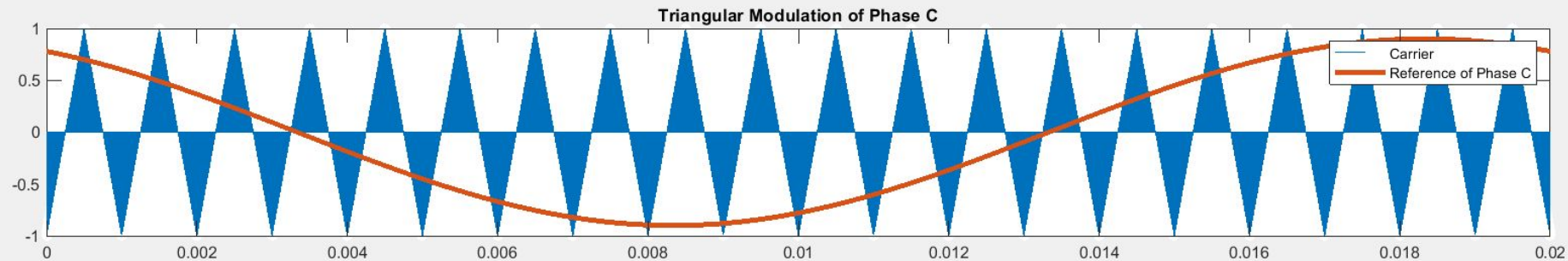

Capacitor current Load Angle with 90

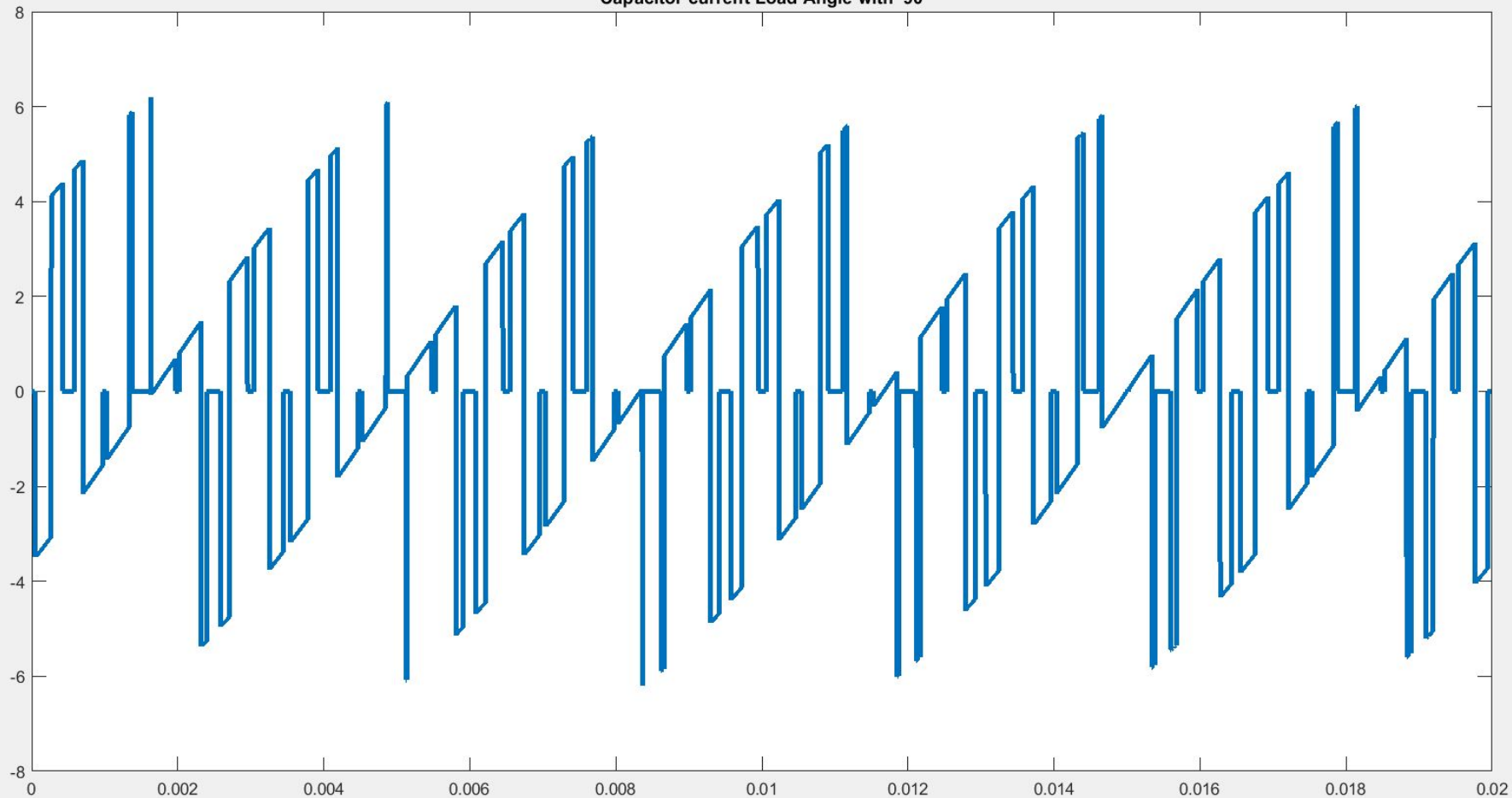

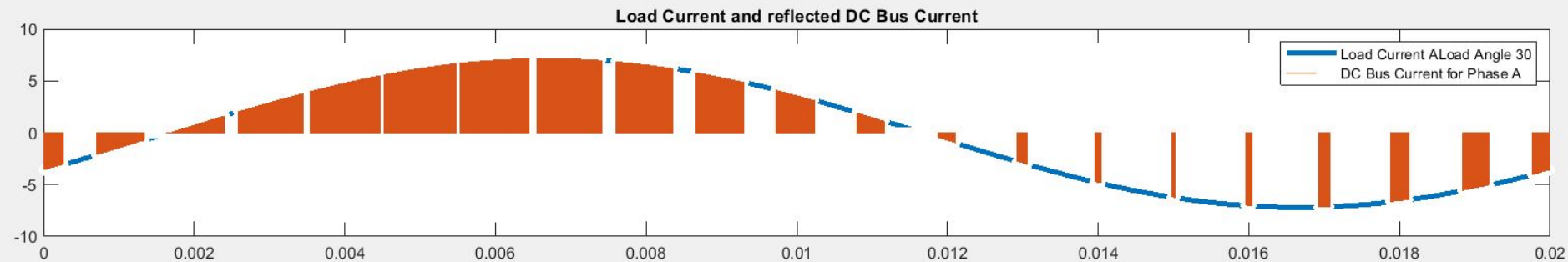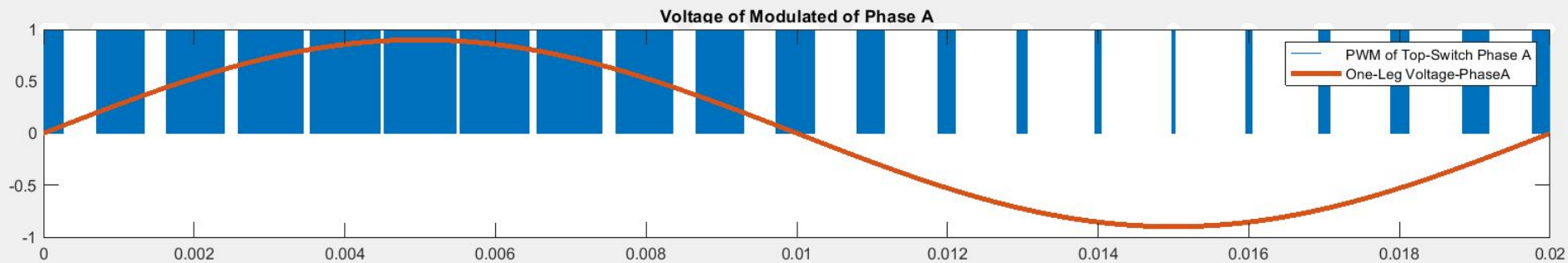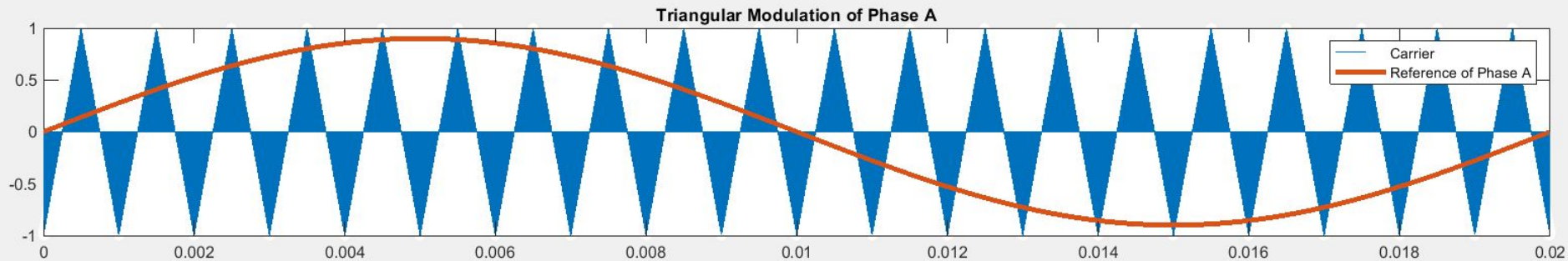

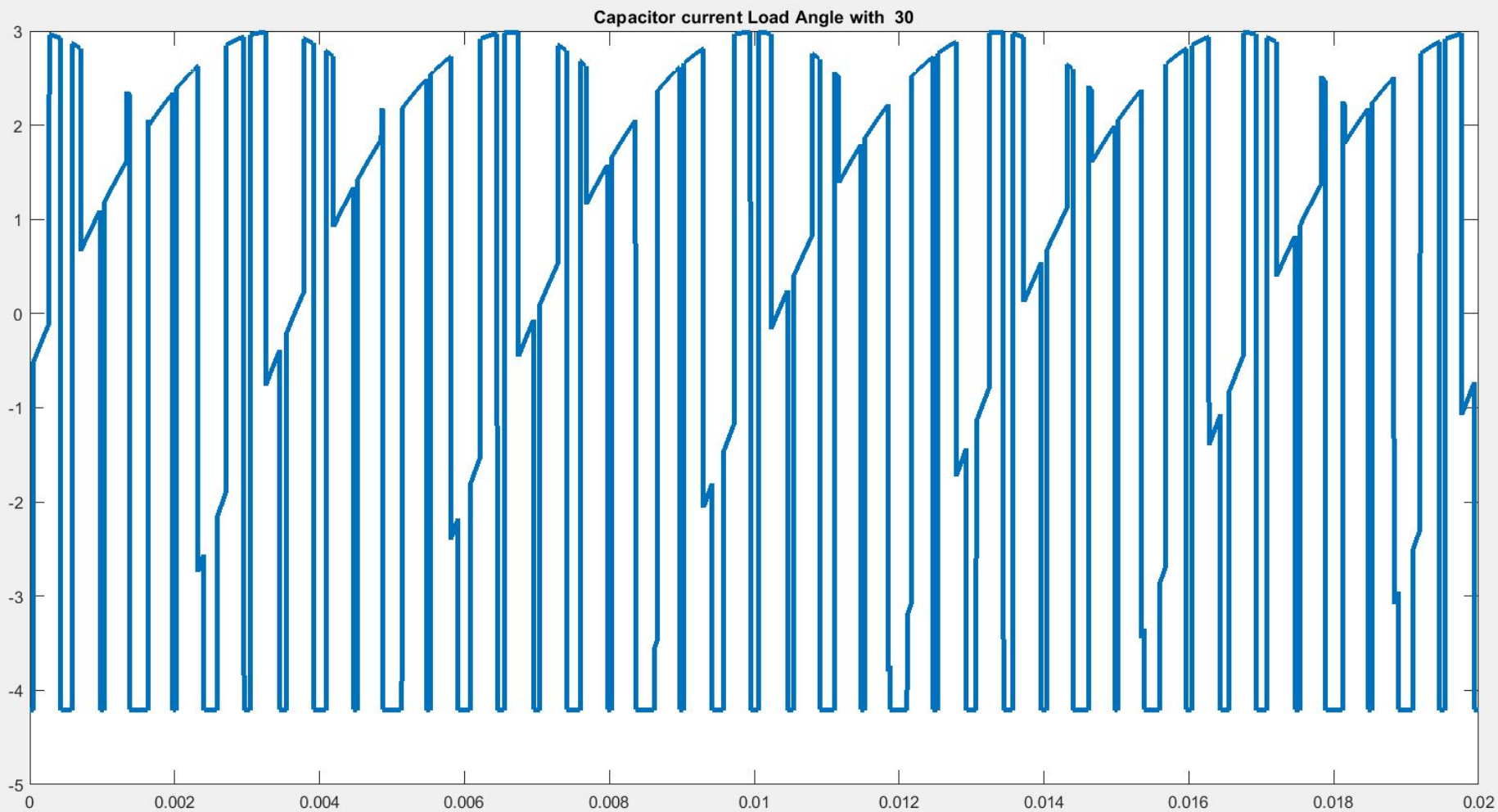


Switching Function

- Switching Function can be written in frequency domain.
- It is converted in time-domain to validate with simulation results.

$$\begin{aligned}
S_a = & \frac{1}{2} + \frac{M}{2} \cos(w_o + \theta_o) + \left(\frac{2}{\pi}\right) \sum_{m=1}^{inf} J_o\left(m\pi \frac{M}{2}\right) \sin\left(m\frac{\pi}{2}\right) \cos(m(w_c + \theta_c)) + \\
& \left(\frac{2}{\pi}\right) \sum_{m=1}^{inf} \sum_{n=-inf}^{inf} \left(\frac{1}{m}\right) J_n\left(\frac{mM\pi}{2}\right) \sin\left(\frac{(m+n)\pi}{2}\right) \cos(m(w_c + \theta_c) + n(\theta_o + w_o))
\end{aligned}$$

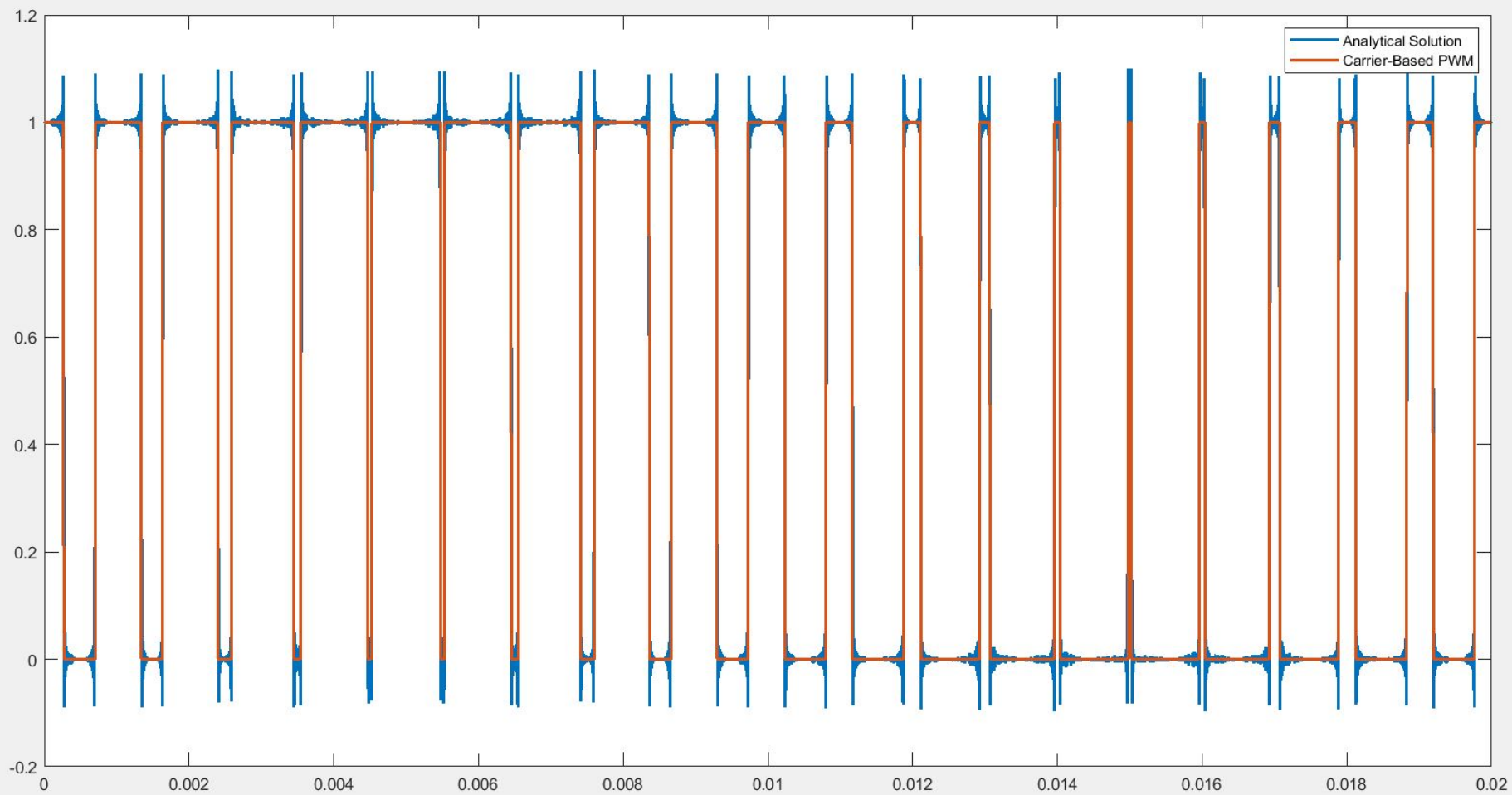Problems

- Frequency components of square wave with sinusoidal duty cycle go to infinity. We can not calculate this, we can restrict our frequencies.
- Gibbs Phenomena, discontinuity (turn-on, turn-off)



- For cosine reference voltage, the reference phase is chosen as $\pi/2$.
- m and n value is restricted by 100.
- we observe ringing

